

FAULT-FINDING CHART FOR MOTORCYCLE CHARGING SYSTEMS

COPYRIGHT © ELECTREX USA 1999




VERY IMPORTANT :
 This fault-finding chart assumes that the user has knowledge of the basics of electricity (Voltage, current, resistance, etc.), and about electrical systems on motorcycles in general. If you do not have this knowledge/experience, find someone that has and let her/him check the charging-system on the bike. The use of this fault-finding chart is entirely at the risk of the user. The author cannot be held responsible for any damage that could arise from the use of this fault-finding chart.

Fully charge the battery. If the battery is not fully charged you may get wrong results using this fault-finding chart. You could just replace it with a battery off another motorcycle that has a good functioning charging-system.

Use an accurate digital multimeter! RR means Regulator/Rectifier. This whole fault-finding chart only works if you have a bike with a combined regulator and rectifier (= regulator/rectifier) in a single case

TAKE NOTICE OF THE FOLLOWING :
 Suzuki used on the older GS models three different colours for the three output-wires of the stator. They were the only manufacturer doing this. The only reason for this can be to cause confusion, because the output of all the three wires is the same. The colours on the wires from the stator are : Yellow, White/blue and White/green. On the Suzuki RR for these models we're talking : Yellow, White/blue and White/red.
JUST THINK THEM ALL BEING YELLOW, and then go on with the tests below

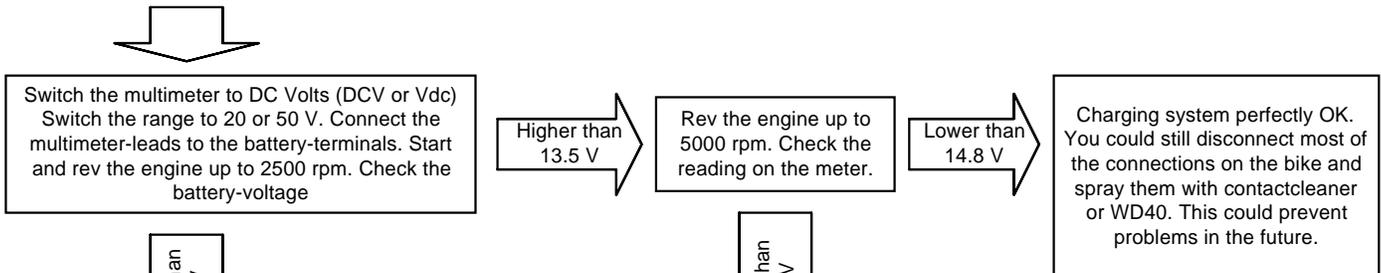

Higher than 13.5 V

Rev the engine up to 5000 rpm. Check the reading on the meter.

Lower than 14.8 V

Charging system perfectly OK. You could still disconnect most of the connections on the bike and spray them with contactcleaner or WD40. This could prevent problems in the future.

Lower than 13.5 V

Higher than 14.8 V

Count the # of different wire-COLOURS emerging from the RR. If there's a yellow wire on a Yamaha RR, don't count it (it is a special output-wire for switching the lights on and off)

More than 4
 Or if there is no RR on the bike at all



4 or less

You've got a permanent magnet alternator system. Let the engine idle, and connect the black multimeter-lead up to the battery(+). Connect the red multimeter-lead up to the red (or white-red = Kawasaki) output wire of the RR. Leave the RR connected up to the bike. Check the reading on the meter. Leave the engine idling !

more than 0.2 V

Bad connection in the positive lead from RR to battery(+). Check the whole lead (suspect the connectors as well as the fuse-box and fuses). Good connections are extremely important in this high current lead. Solve the problem and return to START

Less than 0.2 V

Connect the red multimeter-lead up to the battery(-). Connect the black multimeter-lead up to the negative output of the RR (Honda : Green, Suzuki : Black-white, Yamaha : Black, Kawasaki : black, other brands normally use a black wire). If you can't find a negative output-wire, then the casing of the RR is normally the negative lead to the frame. Check the reading on the meter. Leave the engine idling !

more than 0.2 V

Bad connection in the negative lead from RR to battery(-). Check the whole lead to the battery(-). If the RR doesn't have an output-lead but uses the case as connection to the frame, clean the area where it is bolted and use new screws. Also check the connection between battery(-) and frame. Also suspect the plate on which the RR is mounted (sometimes it is rubbermounted and uses an extra cable from this plate to the battery(-) or frame). Disconnect all suspect terminals and clean. Best solution : connect the RR straight up to the battery(-) with an extra lead. Solve the problem and return to START

less than 0.2 V



B

If you have an RR with 4 different wire-COLOURS emerging from it find the switched +12V supply input. (Normally Honda : BLACK, Suzuki : ORANGE, Yamaha : BROWN, Kawasaki : BROWN, otherwise check the wiring-diagram for the extra wire coming from the ignition-switch). Connect the red multimeter-lead to the battery(+) and the black multimeter-lead to the switched +12V input-wire (the one you just found). Leave the RR fully connected up to the bike and let the engine idle. Switch on the lights. Check the reading on the meter.

more than 0.2 V

Bad connection from the battery(+) through the ignition-switch to the switched +12V supply-input on the RR. Check the whole electrical circuit. This is one of the most difficult faults to find. Suspect the ignition-switch itself, the fuse-box and its connections. The RR thinks the battery-voltage is too low while the actual voltage is correct or too high. Disconnect all terminals and clean them with contact-cleaner. If you have solved the problem, return to START

Reading is lower than 0.2 V

You have LESS than 4 different wire-COLOURS

Stop the engine. Disconnect the wires emerging from the stator. These are usually three yellow (or white = Yamaha) wires. Switch the multimeter to Ohms, the lowest range on the meter. Measure the resistance between all three wires coming from the stator, so you need to take three readings.

One of the readings is lower than 0.5 Ohms or higher than 2 Ohms

All readings are within 0.5 to 2.0 Ohms

Connect one of the multimeter-leads up to one of the three yellow (or white = Yamaha) wires. Connect the other multimeter-lead up to the engine-casing. Check the reading on the meter. Make sure the connection to the casing is a good one !

You have any reading between 100 Ohms and zero Ohms (= 0 Ohms = no resistance !)

Stator is at fault. Replace the stator and return to START

You have no reading at all, or OL in the display

Switch the multimeter AC-Voltage (Range at least to 100 Vac). Make sure you DON'T switch it to DC-Voltage (=DCV or Vdc). Connect the multimeter-leads between two of the three yellow (or white = Yamaha) wires emerging from the stator. Start the engine and rev it up to app. 5000rpm. Check the reading on the meter. Switch one of the multimeter-leads to another yellow (or white) wire and check the reading again. Switch the other multimeter-lead to another yellow (or white) wire, and check the reading again.

The three readings are not equal, or one of them is below 50 Volts (AC)

Three equal readings, all higher than 50 Volts (AC)

Goto

C



Disconnect the RR from the bike. Switch the multimeter to the DIODE-TEST function. (The reading on the display will be in VOLTS now, not in Ohms!) Connect the RED multimeter-lead to the RED (or white/red = Kawasaki) output wire of the RR. Connect the BLACK multimeter-lead to one yellow (or white = Yamaha) wire. Check the reading. Repeat this procedure for the two other yellow wires.

You have a reading of 1.00 V or lower on one of the three tests.

You have a reading of 1.5 V or higher on all three tests

Connect the BLACK multimeter-lead to the red (or white/red = Kawasaki) output wire of the RR. Connect the RED multimeter-lead to one yellow (or white = Yamaha) wire. Check the reading. Repeat this procedure for the two other yellow wires.

You have a reading below 0.2 V or above 1.0 V on one of the three tests

You have a reading on the display around 0.50 V on all three tests

Connect the BLACK multimeter-lead to the negative output wire of the RR (Kawasaki : BLACK, Yamaha : BLACK, Honda : GREEN, Suzuki : BLACK/WHITE). If there is no output wire, connect the black multimeter-lead to the RR-case. Connect the RED multimeter-lead to one yellow (or white = Yamaha) wire. Check the reading. Repeat this procedure for the two other yellow wires.

You have a reading of 1.00 V or lower on one of the three tests.

You have a reading of 1.5 V or higher on all three tests

Connect the RED multimeter-lead to the negative output wire of the RR (Kawasaki: BLACK, Yamaha : BLACK, Honda : GREEN, Suzuki : BLACK/WHITE). If there is no output wire, connect the black multimeter-lead to the RR-case. Connect the BLACK multimeter-lead to one yellow (or white = Yamaha) wire. Check the reading. Repeat this procedure for the two other yellow wires.

You have a reading below 0.2 V or above 1.0 V on one of the three tests

You have a reading on the display around 0.50 V on all three tests

As this was the last test, the only thing that can be at fault is the battery itself. replace it with another fully charged one and return to START

RR is at fault, replace it with a new one and return to START



Is there an RR on the bike ? (somewhere on the frame under the bodywork)

No

You have an integrated generator (car-type, with built in regulator and rectifier). Most of the problems with this kind of generator are bad connections, from generator to battery (battery doesn't charge), or a burned out regulator (battery-voltage too high) Sometimes the generator itself is at fault. You could check the resistance of the fieldwinding (around 5 Ohms) and the state the brushes are in. Otherwise leave it to an expert. After solving the problem, return to START

Yes

Switch the multimeter to DC-Voltage (DCV or Vdc) Range 20 or 50V. Connect the multimeter-leads to the battery-terminals. Start the engine and rev it up to app.5000rpm. Check the voltage-reading.

Higher than 14.8 V

RR at fault. Voltage is not regulated. Replace the RR and return to START

Lower than 14.8 V

Stop the engine. Disconnect the blockconnector to the generator closest to the engine. This connector must have at least three yellow (or white = Yamaha) wires in it and one or two extra ones. Switch the multimeter to the lowest Ohms-range. measure the resistance between the two other wires, or between the single extra one (apart from the yellow ones) and the engine-casing.

You have a reading lower than 3 Ohms or higher than 10 Ohms

The fieldwinding in the generator or the brushes to the rotor are at fault. If there are any brushes inside the generator, disconnect them and measure the resistance between the two copper slip-rings on the rotor. These are the rings on which the brushes run.

(If there are no brushes inside the generator, replace the fieldwinding or if that's not possible separately, replace the whole stator and return to START)

resistance lower than 3 Ohms or higher than 6 Ohms

Rotor at fault. Replace it with a new one, and return to START

Reading between 4 Ohms and 6 Ohms

resistance between 4 Ohms and 6 Ohms

Connect one spare wire to the battery(+) terminal and connect it up to one of the extra wires that are in the blockconnector, apart from the yellow (or white = Yamaha) wires. Connect a second spare wire between the battery(-) and the other extra wire in the connectorblock. If you have only one extra wire, only connect the battery(+) wire to this one. Make sure the battery(-) is still connected to the frame. Switch the multimeter to AC-Volts, range at least 100 V (ACV or Vac). Start the engine and rev it up to app. 5000 rpm. Connect the multimeter-leads up between two of the yellow (or white = Yamaha) wires. Check reading on multimeter. Switch one of the multimeter-leads to another yellow wire and check the reading again. Then switch the other multimeter-lead and check the reading again.

Wiring to the brushes or the brushes themselves at fault. Replace the brushes, check the wiring to the brushes and return to START

The three readings are not equal, or they are below 50 Volts (AC)

Stator at fault. Replace stator and return to START

Three equal readings, all higher than 50 Volts (AC)

Stop the engine. Switch the multimeter to DC-Voltage (DCV or Vdc). With the block-connector disconnected as above, connect the multimeter-leads up to the two extra wires in this connector (apart from the three yellow wires), this in the connector-block emerging from the wiring-loom, not the other side going to the generator. If there's only one extra wire, connect it to one multimeter-lead and connect the other multimeter-lead to the engine-casing. When you switch on the ignition, Check the reading on the display.

No reading or a reading lower than 10 V (DC)

RR at fault. Replace it with a new one and return to START

Reading 10V or higher

